

Wheatstone Bridge Optimization Using Factorial Experiments

Gavin Gray and Christos Anastasiades

1.Circuit Diagram

 


Figure 1: Wheatstone Bridge Circuit Diagram.

Aim: to detect 20 resistors as accurately as possible using a Wheatstone Bridge circuit
Problem: When galvanometer current is between $\pm 0.2\text{mA}$, the indicated value is zero. The resistance change that causes currents in this range to flow therefore cannot be detected.

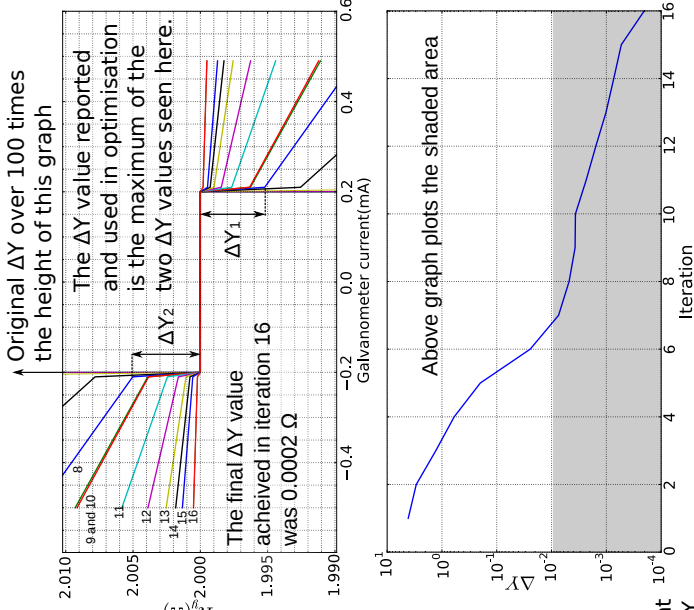


Figure 2: Description of the design at different iterations and the improvements in ΔY .

2.Iterative Design

The iterations were performed by running experiments varying each control factor by, initially, 10%. The result of these experiments was the ΔY value indicated on the right. Using this result it was then possible to regress the input factors into a model using RS/1 and use this model to find optimum values to minimise ΔY .

On each iteration the optimisation would find factors limited at the edges of the range chosen in the experiments. The range chosen for the next experiment was then based on this observation. These ranges were chosen based on intuition - a percentage of the value the factor was found to be limited at.

The graph on the right shows the ΔY achieved on each iteration. This had to be plotted on a logarithmic scale for the higher iterations to be visible.

3.Results

ΔY : Optimisation 1	Power: Optimisation 2
$V_E=33.810\text{ V}$	$V_E=1.500\text{ V}$
$R_A=1.0000\text{ }\Omega$	$R_A=1.0006\text{ }\Omega$
$R_B=1.3413\text{ }\Omega$	$R_B=3.6994\text{ }\Omega$
$R_C=1.2310\text{ }\Omega$	$R_C=7.2199\text{ }\Omega$
$R_D=1.8356\text{ }\Omega$	$R_D=3.9033\text{ }\Omega$
$R_F=1.0002\text{ }\Omega$	$R_F=1.0001\text{ }\Omega$

To obtain the greatest accuracy possible the first set of iterations were simply optimising ΔY without considering any other design objectives. These are illustrated in section 2. The high voltage and low resistance made it an impractical design.

A common battery voltage of 1.5 V was chosen as a reasonable V_E . The power dissipated in each resistor was constrained below 0.1W in subsequent iterations.

Final Chosen Components	Component Tolerances (%)	Component Power rating (mW)	Max.(6 σ) Dissipated power (mW)	Yield (σ)
$V_E=1.500\text{ V}$	N/A(-20)			
$R_A=3.00\text{ }\Omega$	± 1	00	N/A	
$R_B=12.70\text{ }\Omega$	± 1	00	115	
$R_C=40.20+36.0=76.20$	± 1	00	19.2	6.53
$R_D=12.00\text{ }\Omega$	± 1	00	3.1	
$R_F=1.00\text{ }\Omega$	± 1	00	12.4	
Total power=167				

The resulting design had a ΔY of 7 m Ω . Unfortunately, this design required 0.1% resistors to be viable. Only 1% resistors were available from online suppliers in the required sizes.

Setting a yield of 6 σ as a design constraint allowed the design to become viable and the final Monte Carlo test produced a worst case 6 σ ΔY of 70m Ω .

Methods

- Control factor ranges
- Test specifications
- Perform experiment
- Check model fit
- Optimise variables
- Confirmation run

A final experiment is always required to validate the optimised design.

10-50% variation on factors was a safe rule of thumb; below which model accuracy was badly affected.

As an arbitrary number of experiments could be run a cubic model was built using a full factorial experiment to increase accuracy.

Fit of the model can be estimated by the reported R^2 (fit of the model to data) value. This can be improved by applying a y-transform, variance weights or bisquare weights.

R^2 is composed of two square sums of observed and predicted responses:

$$R^2 = \frac{SS_{reg}}{SS_{obs}}$$

Calculations

It was necessary to calculate R_C for each circuit to ensure it would balance at 20. This was achieved in the Python code using the following equations, by asserting R_y at 20.

$$R_C = \frac{R_B \times R_D}{R_y} \quad R_C = \frac{R_B \times R_D}{2}$$

Power dissipation of each resistor and the circuit as a whole was added as a response in the Python code. Thevenin's theorem was applied at node V_x to solve for voltages V_y and V_z . Yield was also added as a additional response, estimating the number of standard deviations able to detect 20.

Statistical Analysis

Using the distrib command it is possible to estimate the effect of resistor tolerances on the model. However, in order to optimise the yield of the circuit easily a Monte Carlo simulator was written in Python. Ideally, this would be run on the model because it involves many experiments.

The region of designs unable to detect a 20 resistor is indicated by shading in the top graph - showing the design after optimisation 2. Optimisation of yield was possible through the same regression model approach as in section 2 by using the Monte Carlo script to output worst case 6 σ values for power dissipation and ΔY . The bottom graph is plotted in the same manner to the top, but for the final design.

For confirmation, a final Monte Carlo was also run.

 


Figure 3: Illustration of the results of Monte Carlo on two optimised designs.

The final circuit is guaranteed to be able to detect a 20 resistor to within 70m Ω , while consuming 167mW when balanced and for a resistor cost of £0.047.